

Ve216 Signals and Systems

Lab 1 Manual


1 Objectives

- Measure the output response of the series RC circuit for a variety of inputs, including a step, a combination of a step and a ramp, and a sinusoid
- Compare results to those computed as part of pre-lab assignment

2 Procedure

Setup

- Function generator: Utility \rightarrow Output Setup \rightarrow Load \rightarrow High Z
- Oscillator: Trigger Menu \rightarrow $\begin{cases} 1. \text{Trigger Mode} \rightarrow \text{Basic} \\ 2. \text{Edge Trigger (Rising Edge)} \\ 3. \text{Trigger Settings} \rightarrow \text{DC Coupling} \end{cases}$
- RC circuit: $R = 1 \text{ K}\Omega$, and $C = 1 \mu\text{F}$

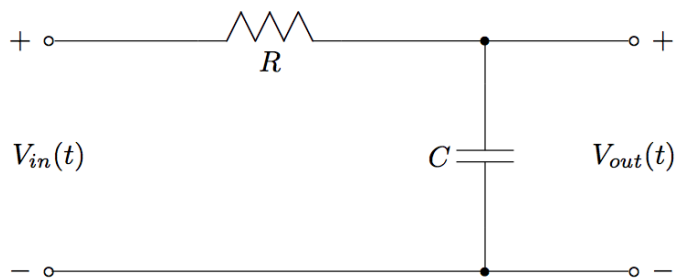

Part 1: Step Response (1 pic + bonus)

- Function generator:
Square wave V_{pp} : 1V frequency: 100Hz
- Oscillator:
CH1: 200mV/div CH2: 200mV/div Time: 2ms
- Bonus: Compare your results with the ideal case

Part 2: Pulse Response (2 pics)

- Function generator: Pulse frequency: 100Hz
 1. Width: 1ms A: 100mV
 2. Width: 0.5ms A: 200mV

Part 3: Ramp Response (1 pic)

- Function generator:
Ramp Vpp: 100mV frequency: 100Hz

Part 4: Sine Response (1 table + bonus)

- Function generator: 10 Vpp

Frequency (Hz)	Vout / Vin	Time Shift	Phase Shift
50			
500			
5k			

- Bonus: Compare your results with ideal case

3 Deliverables

You should submit a post-lab report containing the following:

1. Objectives
2. Experimental results (numerical results, figures)
3. Error analysis, and discussion
4. Conclusion

Each group needs to submit only one report.